
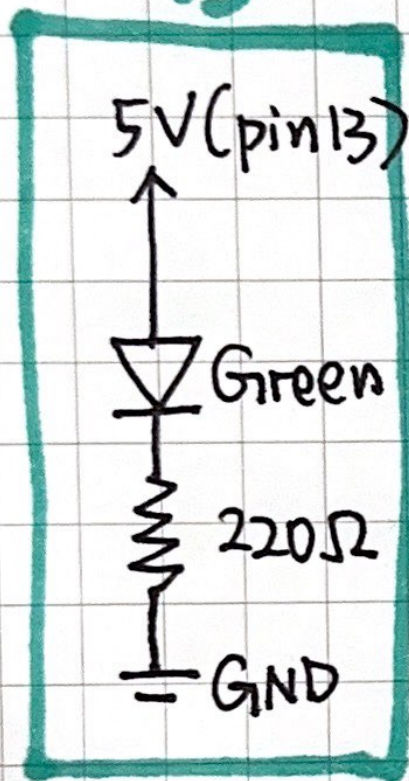



13

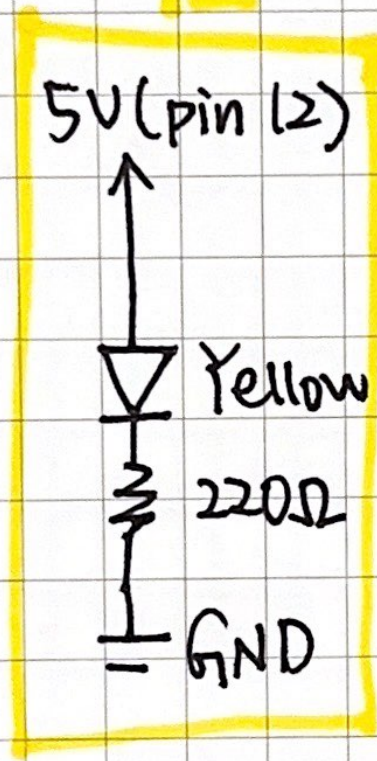

12



11

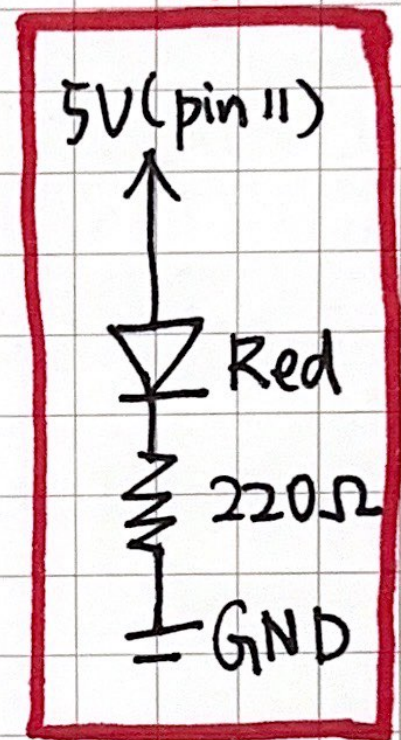

This is the schematic for my blinking project. To make each LED blink independently, I chose to build 3 circuits.

Green, Yellow, Red LEDs all have roughly 1.8V voltage drop. To make my circuits safe and my LEDs bright, I need to calculate minimal resistance I'll need.

$$V = 5V$$

$$V_{\text{drop}} = 1.8V$$

$$V_{\text{circuit}} = 5V - 1.8V = 3.2V$$

$$I = 20\text{mA} \text{ desired current}$$

$$I_{\text{max}} = 30\text{mA}$$

$$V = I \times R$$

$$3.2V = 0.02 \times R$$

$$R = 160\Omega$$

desired

↑

closest to desired resistance.

I choose to use  $220\Omega$  resistor for each circuit.

$$V = I \times R$$

$$3.2V = 0.03 \times R$$

$$R = 107\Omega$$

or above